

Computer-Aided VLSI System Design

Homework 2: Simple MIPS CPU

TA: 林奕廷 r09943017@ntu.edu.tw **Due Tuesday, Oct. 18, 14:00**

TA: 羅宇呈 f08943129@ntu.edu.tw

Data Preparation

- Decompress 1111_hw2.tar with following command

```
tar -xvf 1111_hw2.tar
```


Folder	File	Description
00_TESTBED	inst_mem.vp	Module of instruction memory (protected)
	data_mem.vp	Module of data memory (protected)
	define.v	File of definition
	testbed_temp.v	Testbed template
00_TESTBED/ PATTERN/p*	inst.dat	Pattern of instructions in binary format
	inst_assembly.dat	Corresponding assembly code of the instruction pattern
	data.dat	Pattern of final data in data memory
	status.dat	Pattern of corresponding status
01_RTL	core.v	Your design
	rtl.f	File list
	01_run	NCVerilog command
	99_clean_up	Command to clean temporary data

Introduction


Central Processing Unit (CPU) is one of the most important core in a computer system. In this homework, you are asked to design a simple CPU which consists of a program counter, an ALU, and a register file. The instruction set of the simple CPU is similar to MIPS ISA. Since the files of testbed (inst_mem.v, data_mem.v) are protected, you have to write the testbed by our own to test your design.

Instruction set
 
```
addi $7 $3 4
sub $7 $7 $5
sw $7 $4 8
bne $3 $5 12
lw $6 $0 8
add $7 $6 $2
sw $7 $4 8
eof
```



Block Diagram

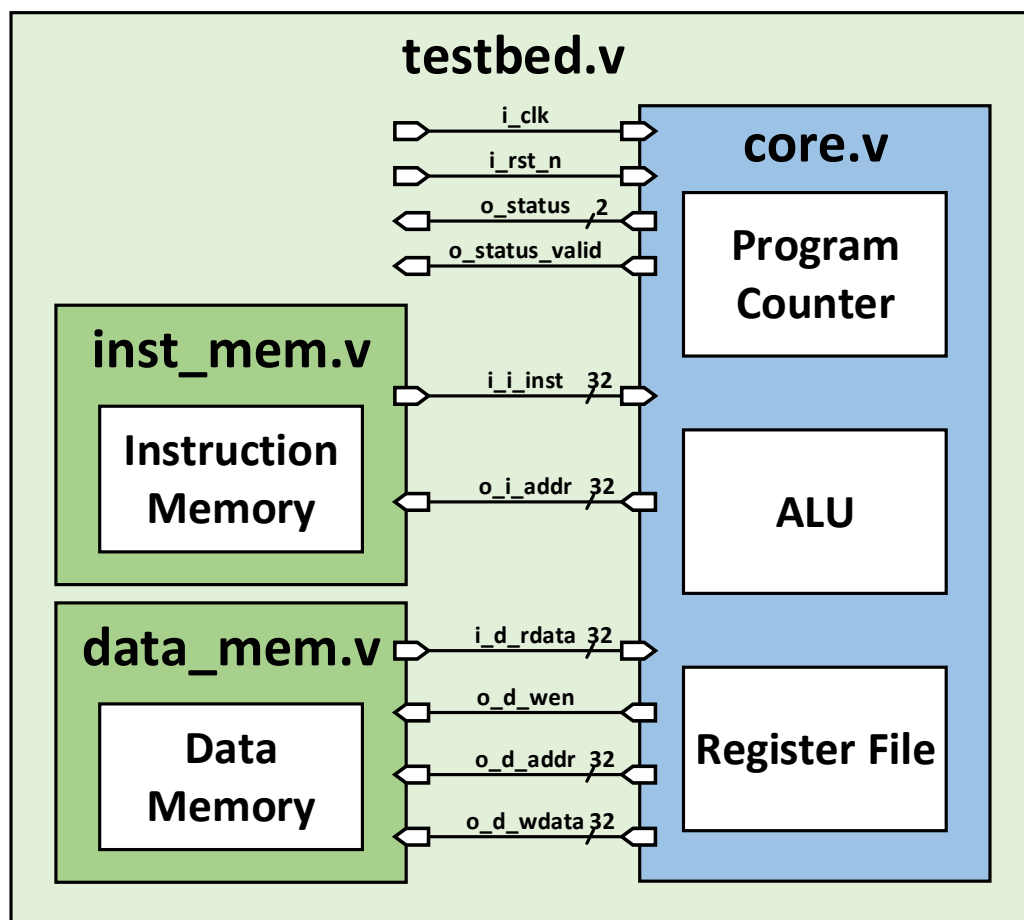

Specifications

1. Top module name: core
2. Input/output description:

Signal Name	I/O	Width	Simple Description
i_clk	I	1	Clock signal in the system.
i_rst_n	I	1	Active low asynchronous reset.
o_i_addr	O	32	Address from program counter (PC)
i_i_inst	I	32	Instruction from instruction memory
o_d_wen	O	1	Write enable of data memory Set low for reading mode, and high for writing mode
o_d_addr	O	32	Address for data memory
o_d_wdata	O	32	Data input to data memory
i_d_rdata	I	32	Data output from data memory
o_status	O	2	Status of the core after processing each instruction
o_status_valid	O	1	Set high if core is ready to output status

3. All outputs should be synchronized at clock **rising** edge.
4. You should set all your outputs and register files to zero when i_rst_n is **low**. Active


low asynchronous reset is used.

5. Instruction memory and data memory are provided. All values in memory are reset to zero.
6. You should create **32-bit registers** in register file.
7. After sending `o_i_addr` to instruction memory, the core can receive the corresponding `i_i_inst` at the next rising edge of the clock.
8. To load data from the data memory, set `o_d_wen` to **0** and `o_d_addr` to relative address value. `i_d_rdata` can be received at the next rising edge of the clock.
9. To save data to the data memory, set `o_d_wen` to **1**, `o_d_addr` to relative address value, and `o_d_wdata` to the written data. At the next rising edge of the clock, the data is written to memory.
10. Your `o_status_valid` should be set to **high** for only **one cycle** for every `o_status`.
11. The testbed will get your output at negative clock edge to check the `o_status` if your `o_status_valid` is **high**.
12. When you set `o_status_valid` to **high** and `o_status` to **3**, stop processing. The testbed will check the data in data memory with golden data.
13. If overflow happened, stop processing and raise `o_status_valid` to **high** and set `o_status` to **2**. The testbed will check the data in data memory with golden data.
14. **Less than 1024** instructions are provided for each pattern.
15. The whole processing time can't exceed **120000** cycles.

Design Description

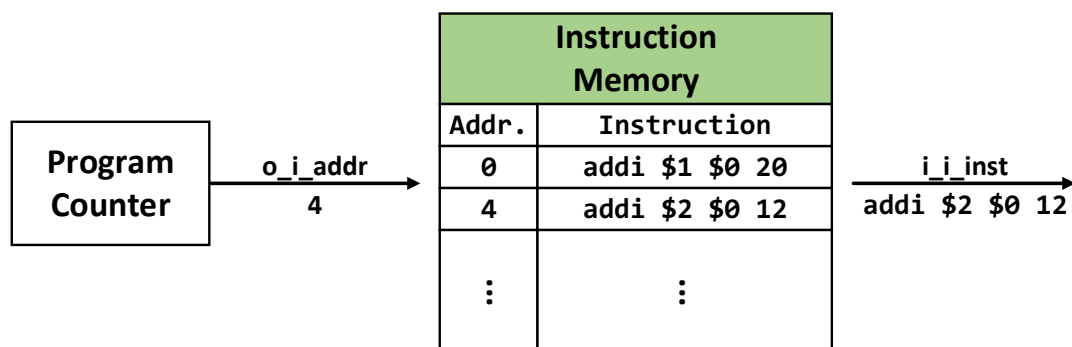1. Program counter is used to control the address of the instruction memory.

$\$pc = \$pc + 4$ for every instruction (except for **beq**, **bne**)



2. Register file contains 32 registers (each register is 32-bit) for operation.

3. Instruction mapping:

a. R-type

[31:26]	[25:21]	[20:16]	[15:11]	[10:0]
opcode	\$s2	\$s3	\$s1	Not used
31				0

b. I-type

[31:26]	[25:21]	[20:16]	[15:0]
opcode	\$s2	\$s1	im
31			0

c. EOF

[31:26]	[25:0]
opcode	Not used
31	0

4. The followings are the instructions you need to design for this homework:

Operation	Assembly	Opcode	Type	Meaning	Note
Add	add	6'd1	R	$\$s1 = \$s2 + \$s3$	Signed operation
Subtract	sub	6'd2	R	$\$s1 = \$s2 - \$s3$	Signed operation
Add unsigned	addu	6'd3	R	$\$s1 = \$s2 + \$s3$	Unsigned operation
Subtract unsigned	subu	6'd4	R	$\$s1 = \$s2 - \$s3$	Unsigned operation
Add immediate	addi	6'd5	I	$\$s1 = \$s2 + im$	Signed operation
Load word	lw	6'd6	I	$\$s1 = Mem[\$s2 + im]$	Unsigned operation
Store word	sw	6'd7	I	$Mem[\$s2 + im] = \$s1$	Unsigned operation
AND	and	6'd8	R	$\$s1 = \$s2 \& \$s3$	Bit-wise
OR	or	6'd9	R	$\$s1 = \$s2 \$s3$	Bit-wise
NOR	nor	6'd10	R	$\$s1 = \sim(\$s2 \$s3)$	Bit-wise
Branch on equal	beq	6'd11	I	if($\$s1 == \$s2$), $\$pc = \$pc + 4 + im$;	PC-relative; Unsigned

				else, \$pc = \$pc + 4	operation
Branch on not equal	bne	6'd12	I	if(\$s1!=\$s2), \$pc = \$pc + 4 + im; else, \$pc = \$pc + 4	PC-relative; Unsigned operation
Set on less than	slt	6'd13	R	if(\$s2<\$s3), \$s1 = 1; else, \$s1 = 0	Signed operation
End of File	eof	6'd14	EOF	Stop processing	Last instruction in the pattern

Note: Use two's complement arithmetic for signed operations.

5. Interface of instruction memory (size: 1024×32 bit)

- i_add[11:2] for address mapping in instruction memory.

```
module inst_mem (
    input          i_clk,      // 1-bit
    input          i_rst_n,    // 1-bit
    input [ 31 : 0 ] i_addr,    // 32-bit
    output [ 31 : 0 ] o_inst    // 32-bit
);
```

6. Interface of data memory (size: 64×32 bit)

- i_add[7:2] for address mapping in data memory,
- To fetch data of data memory in your **testbed** (not in your RTL code!), use the following instance name.

```
u_data_mem.mem_r[i]
```

```
module data_mem (
    input          i_clk,      // 1-bit
    input          i_rst_n,    // 1-bit
    input          i_wen,      // 1-bit
    input [ 31 : 0 ] i_addr,    // 32-bit
    input [ 31 : 0 ] i_wdata,   // 32-bit
    output [ 31 : 0 ] o_rdata   // 32-bit
);
```

7. Overflow may happen

- **Situation1**: Overflow happens at arithmetic instructions (add, sub, addu, subu, addi).
- **Situation2**: The address of data/instruction memory is out of the memory size (Do not consider the case if instruction address is beyond eof, but the address mapping is still in the size of instruction memory).

Once an overflow happens, the testbed stops and checks the data memory.

8. 4 types of o_status:




o_status[1:0]	Definition
2'd0	R_TYPE_SUCCESS
2'd1	I_TYPE_SUCCESS
2'd2	MIPS_OVERFLOW
2'd3	MIPS_END

9. Last instruction would be eof for every pattern.


10. There is no unknown opcode in the pattern.

Sample Waveform

1. Status check

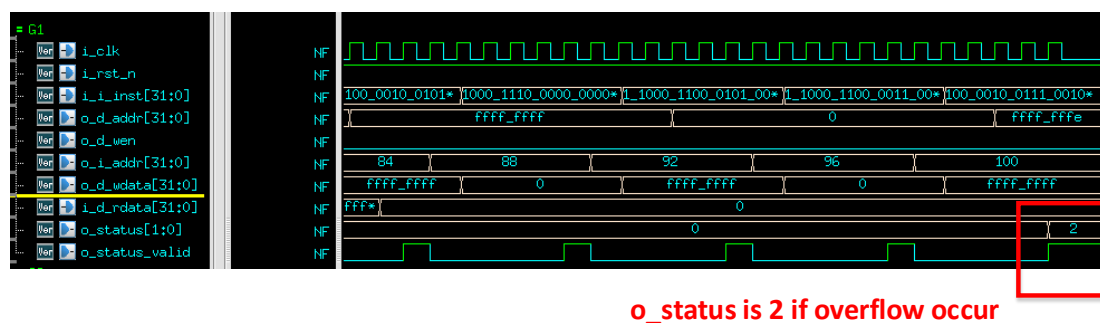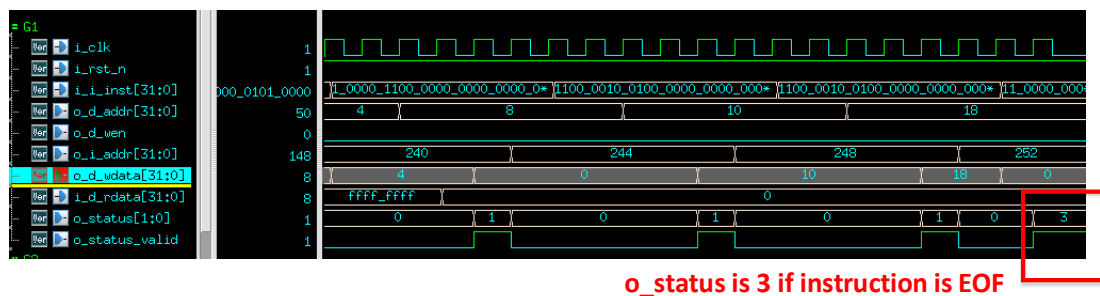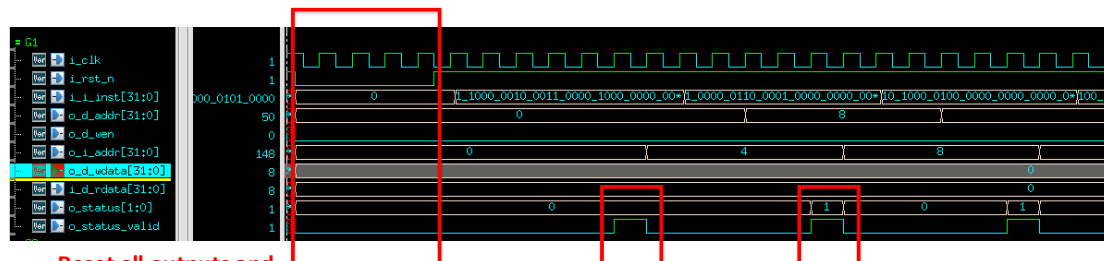


 2. Read instruction from instruction memory




Output `o_i_addr` for relative instruction → Get `i_i_inst` at the next rising edge of clock

3. Load data from data memory

 

`o_d_wen` = 0, load data from data memory at `o_d_addr` = 24 → Receive `i_d_rdata` at next rising edge of clock

4. Save data to data memory

 

`o_d_wen` = 1, store `o_d_wdata` to data memory at `o_d_addr` = 4 →

Testbed

1. Things to add in your testbed

- Clock
- Reset
- Waveform file (.fsdb)
- Function test
- ...

Submission

1. Create a folder named **studentID_hw2**, and put all below files into the folder:

- **rtl.f** (your file list)
- **core.v**
- **all other design files** in your file list (optional)

Note: Use **lower case** for the letter in your student ID. (Ex. r09943017_hw2)

2. Compress the folder **studentID_hw2** in a **tar file** named **studentID_hw2_vk.tar** (*k* is the number of version, *k* = 1, 2, ...)

```
tar -cvf studentID_hw2_vk.tar studentID_hw2
```

TA will only check the last version of your homework.

Note: Use lower case for the letter in your student ID. (Ex. r09943017_hw2_v1)

3. Submit to NTU COOL

Grading Policy

1. TA will run your code with following format of command. Make sure to run this command with no error message.

```
ncverilog -f rtl.f +define+p0 +access+rw
```

2. Pass the patterns to get full score.
 - Provided pattern: **80%** (patterns: p0, p1)
 - **40%** for each pattern (data in data memory: **20%**, status check: **20%**)
 - **Don't implement the answers in your design directly!**
 - Hidden pattern: **20%** (20 patterns in total)
 - **1%** for each pattern (data & status both correct)
3. Delay submission:
 - In one day: **(original score)*0.6**
 - In two days: **(original score)*0.3**
 - More than two days: **0 point** for this homework
 - Lose **3 point** for any wrong naming rule

Hint

1. Design your FSM with following states
 - Idle
 - Instruction Fetching
 - Instruction decoding
 - ALU computing/Load data
 - Data write-back
 - Next PC generation
 - End of processing