

Computer-Aided VLSI System Design

Homework 1: Arithmetic Logic Unit

TA: 陳定揚 r09943115@ntu.edu.tw **Due Tuesday, Oct. 4th, 13:59**

TA: 羅宇呈 f08943129@ntu.edu.tw

Data Preparation

- Decompress 1111_hw1.tar with following command


```
tar -xvf 1111_hw1.tar
```

Files/Folder	Description
alu.v	Your design
testbench.v	File to test your design
pattern/	9 instruction data for testing
01_run	NCverilog simulation command
09_clean	Command for cleaning temporal files

Introduction

The Arithmetic logic unit (ALU) is one of the components of a computer processor. In this homework, you are going to design an ALU being able to compute special operations

Block Diagram

 

Specifications

1. Top module name: alu
2. Input/output description:

Signal Name	I/O	Width	Simple Description
i_clk	I	1	Clock signal in the system
i_rst_n	I	1	Active low asynchronous reset
i_valid	I	1	The signal is high if input data is ready
i_data_a	I	8	Signed input data with 2's complement representation (3b integer + 5b fraction)
i_data_b	I	8	
i_inst	I	3	Instruction for ALU to operate
o_valid	O	1	Set high if ready to output result
o_data	O	8	Result after ALU processing with 2's complement representation (3b integer + 5b fraction).

3. All inputs are synchronized with the negative edge clock.
4. All outputs should be synchronized at clock **rising** edge (Flip-flops are added at outputs)
5. Active low asynchronous reset (You should set all your outputs to be zero when i_rst_n is **low**)
6. i_valid will be pulled **high** for one cycle for ALU to get i_data_a, i_data_b and i_inst
7. i_valid will be pulled **high** anytime
8. o_valid should be pulled **high** for only **one cycle** for every o_data
9. When o_valid is **high**, the testbench will get your output at negative clock edge to check the answer
10. You can raise your o_valid anytime. TA will check your answer when o_valid is high


Design Description

1. The followings are the functions of instructions you need to design for this homework:

i_inst [2:0]	Operation	Description
000	Signed Addition	$o_data = i_data_a + i_data_b$
001	Signed Subtraction	$o_data = i_data_a - i_data_b$
010	Signed Multiplication	$o_data = i_data_a * i_data_b$
011	NAND	$o_data = (i_data_a \cdot i_data_b)'$
100	XNOR	$o_data = (i_data_a \oplus i_data_b)'$
101	Sigmoid	$o_data = \sigma(i_data_a)$
110	Right Circular Shift	See 111_HW1_note.pdf
111	Min	$o_data = \min(i_data_a, i_data_b)$ If $i_data_a = i_data_b$, $o_data = i_data_a$

2. Considerations between digital systems and signals:
- Bit-wise operation for instruction 011 and 100.
 - For instruction 000, 001 and 010, output value might exceed the range of 8b representation (3b integer + 5b fraction).
 - For instruction 000, 001 and 010, if the output value exceeds the maximum value of 8b representation, use the **maximum value** as output, and vice versa.
 - For instructions 010, the result need to be **rounded to nearest number** before output
 - For instructions 101, you need to implement a sigmoid function which is a popular activation function in an artificial neural network. In order to have a easier implementation, we use **piecewise linear approximation** to compute sigmoid function. You can check 111_HW1_note.pdf for details.
 - For instruction 110, you should implement **right circular shift** function and view i_data_b as rotation amount (8b integer). You can check 111_HW1_note.pdf for details.
 - For instruction 111, if $i_data_a = i_data_b$, just output i_data_a
 - Before and after the operation, if the total number of bits of the variable (reg or wire) is inconsistent, the system presets to complement the zero extension. Please use sign extension for the signal at the appropriate time.
 - For fixed-point operation, please pay attention to the position of separation between integer and fraction after ALU operation.

Sample Waveform

 

Running RTL Simulation

1. To obtain file permissions for the entire folder have read/write/execute, run the following command under ./1111_hw1 before running simulation

```
chmod -R 777 ./
```

2. To run RTL simulation, you can execute 01_run directly

```
./01_run
```

3. To clean temporal file after simulation

```
./09_clean_up
```

Submission

1. Create a folder named **studentID_hw1**, and put all below files into the folder
 - alu.v

Note: Use lower case for the letter in your student ID. (Ex. r09943115_hw1)

2. Compress the folder **studentID_hw1** in a **tar file** named **studentID_hw1.tar**

```
tar -cvf studentID_hw1.tar studentID_hw1
```

3. Submit to NTU Cool

Grading Policy

1. TA will run your code with following format of command. Make sure to run this command with no error message

```
ncverilog testbench.v alu.v +define+ALL +access+rw
```

2. Pass all the instruction test to get full score

- Released patterns: **80%**

i_inst [2:0]	Operation	Score
000	Signed Addition	10%
001	Signed Subtraction	10%
010	Signed Multiplication	10%
011	NAND	5%
100	XNOR	5%
101	Sigmoid	20%
110	Right Circular Shift	10%
111	Min	10%

- Hidden pattern: **20%**
 - Hidden pattern contains 9 different instructions
 - Only if you pass all patterns will you get full 20% score-

3. Delay submission

- In one day: **(original score)*0.6**
- In two days: **(original score)*0.3**
- More than two days: **0 point** for this homework

4. Lose **3 point** for any wrong naming rule

References

1. 2's complement:
https://en.wikipedia.org/wiki/Two%27s_complement
2. To understand fixed-point representation with fraction number:
<https://reurl.cc/D3xQnR>